



Table of Contents

Chapter 3 Basic Electrical Circuits

Unit 10 Series Circuits	115
Introduction.....	115
10.1 Practical Uses of the Series Circuit.....	115
Lighting.....	115
Control Circuit.....	116
Signaling Circuit.....	116
Internal Equipment Wiring.....	116
10.2 Understanding Series Calculations.....	116
Resistance.....	116
Voltage.....	116
Kirchoff's Voltage Law.....	117
Kirchoff's Current Law.....	118
Power.....	119
10.3 Series Circuit Calculations.....	119
10.4 Power Calculations.....	120
10.5 Variations.....	120
10.6 Series Circuit Notes.....	120
10.7 Series-Connected Power Supplies.....	120
Unit 10 – Summary.....	121
Unit 10 – Conclusion.....	122
Unit 10 – Practice Questions.....	123
Unit 11 Parallel Circuits	125
Introduction.....	125
11.1 Practical Uses.....	125
Receptacle.....	125
Lighting.....	125
Other Uses.....	125
11.2 Understanding Parallel Calculations.....	126
Voltage.....	126
Kirchoff's Current Law.....	126
Power.....	127
11.3 Circuit Resistance.....	127
Equal Resistance Method.....	128
Product-Over-Sum Method.....	128
Reciprocal Method.....	129

11.4 Parallel Circuit Notes.....	129
11.5 Parallel-Connected Power Supplies.....	130
Unit 11 – Summary.....	131
Unit 11 – Conclusion.....	132
Unit 11 – Practice Questions.....	133
Unit 12 Series-Parallel Circuits	135
Introduction.....	135
12.1 Review of Series and Parallel Circuits.....	135
Series Circuit Review.....	135
Parallel Circuit Review.....	135
12.2 Working Series-Parallel Circuits.....	136
12.3 Voltage.....	137
12.4 Current.....	137
Unit 12 – Summary.....	138
Unit 12 – Conclusion.....	138
Unit 12 – Practice Questions.....	139
Unit 13 Multiwire Circuits	141
Introduction.....	141
13.1 Neutral Conductor.....	141
13.2 Grounded Conductor.....	141
13.3 Current Flow on the Grounded (Neutral) Conductor.....	142
2-Wire Circuit.....	142
3-Wire 120/240V 1Ø Circuit.....	142
13.4 Balanced Systems.....	143
13.5 Unbalanced Current.....	143
3-Wire 120/240V 1Ø Circuit.....	143
3-Wire Circuit from a 4-wire 3Ø System.....	143
4-Wire, 3Ø Circuit.....	144
13.6 Multiwire Branch Circuit.....	144
2-Wire Circuit Voltage Drop.....	144
Multiwire Circuit Voltage Drop.....	145
13.7 Dangers of Multiwire Circuits.....	145
Fire Hazard.....	146
Destruction of Equipment as Well as Fire Hazard.....	146
13.8 NEC Requirements.....	147
Unit 13 – Summary.....	148

Unit 13 – Conclusion	149		
Unit 13 – Practice Questions	150		
Chapter 3 – Final Review Questions	153		
Chapter 4			
Electrical Systems and Protection			
Unit 14 The Electrical System	159		
Introduction	159		
14.1 Current Flow	159		
14.2 Utility Neutral Current Path	159		
Multipoint Neutral Ground	159		
14.3 Utility Ground-Fault Current Path	160		
14.4 Premises Neutral Current Path.....	160		
Single Point Neutral Bond	160		
14.5 Premises Ground-Fault Current Path.....	160		
Earth as Ground Fault Path for Systems 600V or Less	161		
14.6 Utility High-Voltage Transmission Lines.....	161		
14.7 Conductor Voltage Drop	161		
14.8 Conductor Power Loss	162		
Current.....	162		
14.9 Reducing Voltage Drop and Power Loss	162		
138 kV Transmission Line	162		
14.10 Generating Plants	163		
14.11 Step-Up Substation at Generating Plant.....	163		
14.12 Transmission Line	163		
14.13 Step-Down Substation	163		
14.14 Primary Distribution Feeders.....	163		
14.15 Distribution Transformer.....	164		
14.16 Secondary Distribution Line	164		
Unit 14 – Summary	165		
Unit 14 – Conclusion	166		
Unit 14 – Practice Questions	167		
Unit 15 Protection Devices	171		
Introduction.....	171		
Part A – Overcurrent Protection Devices	171		
15.1 Overcurrent Protection	171		
Overload	171		
Ground Fault	171		
Short Circuit.....	172		
15.2 Clearing Faults	172		
Time – Current Curves.....	172		
Remove Dangerous Touch Voltage.....	172		
15.3 Overcurrent Protection Device Types	172		
15.4 Fuse.....	173		
Construction.....	173		
Overload Protection.....	173		
			Short-Circuit and Ground-Fault Protection 173
15.5 Circuit Breaker Trip Elements.....	173		
Thermal Trip Element.....	173		
Magnetic Trip Element	173		
15.6 Circuit Breaker Types	174		
Inverse Time	174		
Adjustable-Trip.....	174		
Instantaneous-Trip	174		
15.7 Available Short-Circuit Current.....	174		
15.8 Interrupting Rating	175		
15.9 Short-Circuit Current Rating.....	175		
15.10 Current Limiting Protection	176		
Part B – Ground-Fault Circuit Interrupters	176		
15.11 How a GFCI Works	176		
15.12 Neutral-to-Case Detection	177		
15.13 Line-to-Neutral Shock Hazard.....	177		
15.14 GFCI Fails – Circuit Remains Energized	177		
15.15 GFCI Test Button	178		
Part C – Arc-Fault Circuit Interrupter	178		
15.16 Arcing Definition	178		
15.17 Series Versus Parallel Arc	179		
Series Arc	179		
Parallel Arc.....	179		
15.18 AFCI and the NEC.....	179		
15.19 AFCI – How They Operate.....	179		
Part D – Ground-Fault Protection of Equipment	180		
15.20 Ground-Fault Protection of Equipment Definition	180		
Unit 15 – Summary	181		
Unit 15 – Conclusion	183		
Unit 15 – Practice Questions	184		
Chapter 4 – Final Review Questions	189		